

Circuits Review

Practice Test Answers:

1. 0.15Ω
2. $7.4V$
3. $2.74W$
4. $82mA$
5. $2.4 \times 10^5 W$
6. $30C$
7. $0.43m\Omega$
8. $20V$
9. 2.0Ω

3

Handwritten calculations:

$$R_T = ?$$

$$\frac{1}{R_T} = \frac{1}{27} + \frac{1}{36}$$

$$R_{T_1} = 15.43\Omega$$

$$R_T = 3.5 + 48 + 15.43 = 66.9$$

$$I = \frac{V}{R_T} = \frac{16V}{66.9} = 0.238A$$

$$P = I^2 R = (0.238)^2 (48)$$


7.1411

$$P = I^2 R = \boxed{2.74 \text{ W}}$$

4 $15 \text{ V} = 6.8 \text{ V} + V_2$

$$V_2 = 8.2 \text{ V}$$
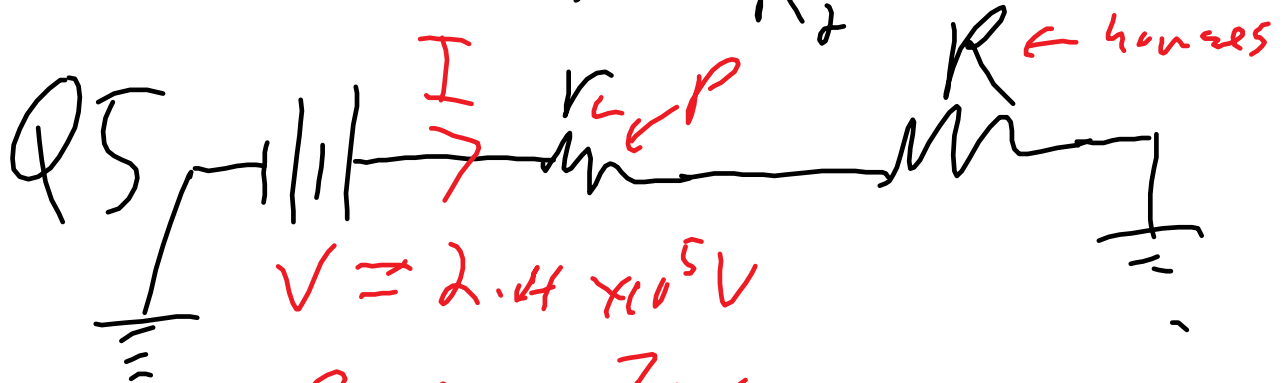
$$I_2 = \frac{V_2}{R_2} = \frac{8.2 \text{ V}}{100 \Omega}$$



$$P = 8.5 \times 10^7 \text{ W}$$

$$P = VI \quad I = \frac{8.5 \times 10^7}{2.4 \times 10^5}$$

$$P_L = I^2 r$$

Q8 $P = \boxed{I^2} r$

$$P_1 = 0.50 \text{ W} = I^2 (250 \Omega)$$

$$I = \sqrt{\frac{0.5}{250}} \approx 0.0447 \text{ A}$$

$$V = I R_T = 0.0447 \text{ A} (450)$$

$$\frac{1}{300} + \frac{1}{600} = \frac{1}{R_{T1}} \quad \text{or} \quad R_{T1} \approx 200$$

$$R_T = 200 + 250$$

$$V = 2015 \text{ V}$$

Q1 0.15Ω

Q2 7.4 V

Q3 2.74 W

Q4 0.082 A

Q5 $2.4 \times 10^5 \text{ W}$


Q6 30 C

Q7 $0.43 \text{ m}\Omega$

Q8 20 V

Q9 2.0Ω

Q3, 7, 8, 9

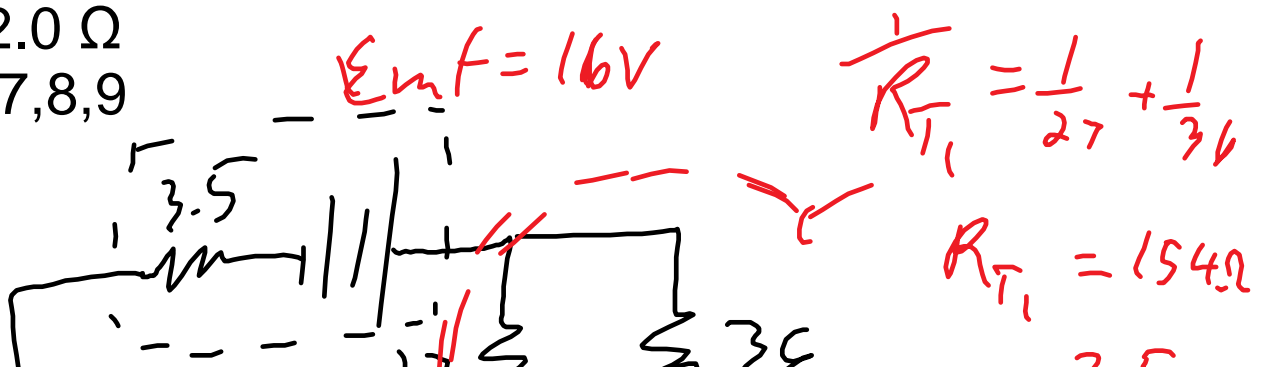




$$P = I^2 R$$

$$I = \frac{V}{R_T} = \frac{16}{66.9} \leftarrow 66.9$$

$$= 0.239 A$$


$$P = (0.239)^2 (48) = \boxed{2.74 W}$$

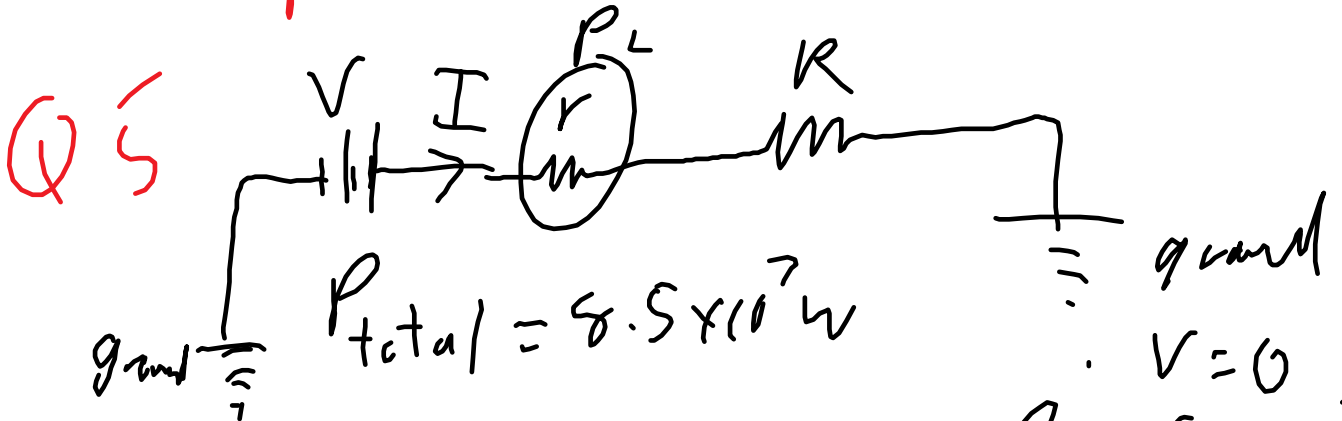

$$V = 0$$

$$P_L = I^2 r \quad I = \frac{P}{V} = \frac{8.5 \times 10^7}{2.4 \times 10^5} = 354 A$$
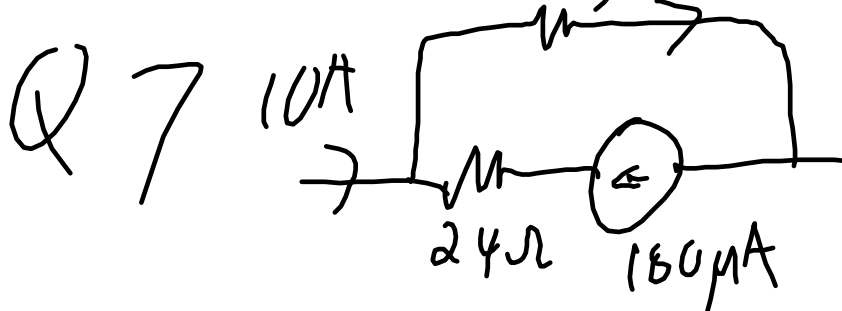
$$P_L = 354^2 (1.9 \Omega) = 2.4 \times 10^5 W$$



$$R_S I_S = R_L I_L$$

$$R_S = \frac{24 (180 \mu A)}{11 A}$$

$$= 430 \mu\Omega$$

$$4.3 \times 10^{-4} \Omega$$

Q8 - Trick -
which R dissipates
the most P? $P = I^2 R$

R_1

$$0.50W = I^2 (250\Omega)$$

$$I = \sqrt{\frac{0.5}{250}} = 0.0447 \text{ A}$$

$$V = I R_T \quad \frac{1}{R_T} = \frac{1}{300} + \frac{1}{600}$$

$$R_T = 200\Omega$$

$$R_T = 250 + 200 = 450$$

$$V = 0.0447 \times 450 = \underline{\quad}$$

Q9

$$P_i = 50W = I_i^2 r$$

$$P_o = 200W = I_o^2 r$$

... $T^{\frac{1}{4}}$

$V_a -$

$$\frac{200}{50} = \frac{I_a \cdot 4}{I_1 \cdot 2}$$

$$V = IR \quad I_a = 2I_1$$

$$60 = I_1(10+r) \quad 60 = I_a(4+r)$$

$$\frac{60}{4+r} = 2I_1 = \frac{2(60)}{10+r}$$

$$10+r = 2(4+r)$$

$$10+r = 8+2r$$

$$\boxed{V = 2\Omega}$$

Practice Test

Q1 0.15Ω

Q2 $7.4V$

Q3 $2.7W$ *

Q4 $0.082A$

Q5 $2.4 \times 10^5 W$

Q6 $30C$

Q7 $4.3 \times 10^{-4}\Omega$

Q8 $20V$

$$\frac{1}{R_{T1}} = \frac{1}{27} + \frac{1}{36}$$

$= 15.4$

Q7 $4.5 \times 10^{-2} \Omega$

Q8 20V

Q9 2.0Ω



$$P = IV = \frac{V^2}{R_T} \quad I = \frac{V}{R_T}$$


$$R_T = 3.5 + 48 + 15.4 = 66.9$$

$$I = \frac{16}{66.9} = 0.24 \text{ A}$$

$$P = (0.24)^2 (48) = 2.74 \text{ W}$$

$$P = 8.5 \times 10^{-7} \text{ W}$$

Q5

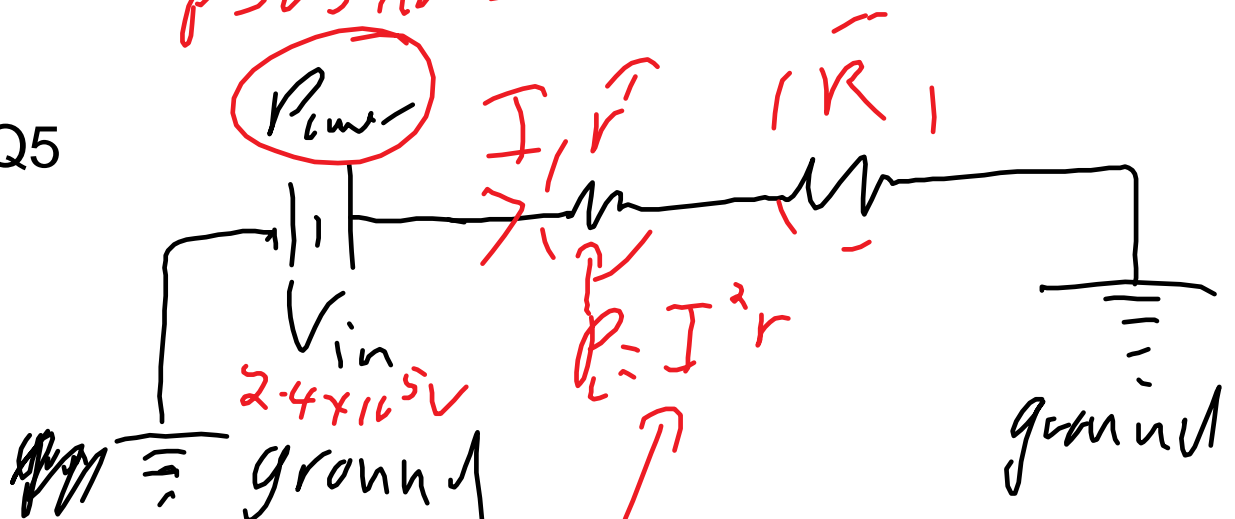

$$T = P \quad 8.5 \times 10^{-7} - 2.53 \text{ A}$$

$$I = \frac{P}{V} = \frac{8.5 \times 10^7}{2.4 \times 10^5} = 353 \text{ A}$$

$$P_L = (353)^2 (1.9) = \boxed{2.4 \times 10^8 \text{ W}}$$

Q6 $I = \frac{Q}{t} = \frac{P}{V}$ $Q = \frac{P \cdot t}{V}$

$$P = IV$$

$$Q = \frac{30 \times 15}{15} = \boxed{30 \text{ C}}$$

Q8

The max power output is 0.5W, this doesn't mean all the resistors are using 0.5W, just one. Which one?

$P = I^2 R$ so R_1 has the most current (series with the battery) so it will be the limiting resistor.

$$0.5 \text{ W} = I^2 (250)$$

$$I = \sqrt{0.5/250} = 0.0447213595499958$$

$$V = IR_t$$

$$1/R_{t1} = 1/300 + 1/600 \quad R_{t1} = 200 \Omega$$

$$R_t = 200 + 250 = 450 \Omega$$

$$V = 450 \times 0.0447213595499958 = 20.12461179749812$$

$$V=20V$$

